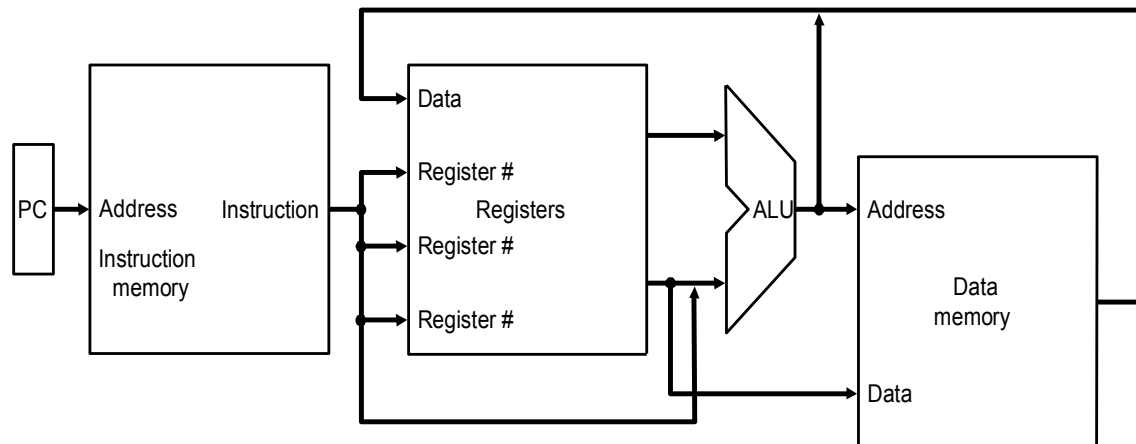


The Processor: Datapath

Implementing MIPS: the Fetch/Execute Cycle

- High-level abstract view of *fetch/execute* implementation
 - use the program counter (PC) to read instruction address
 - *fetch* the instruction from memory and increment PC
 - use fields of the instruction to select registers to read
 - *execute* depending on the instruction
 - repeat...





Overview: Processor Implementation Styles

- Single Cycle
 - perform each instruction in 1 clock cycle
 - clock cycle must be long enough for slowest instruction; therefore,
 - disadvantage: only as fast as slowest instruction
- Multi-Cycle
 - break fetch/execute cycle into multiple steps
 - perform 1 step in each clock cycle
 - advantage: each instruction uses only as many cycles as it needs
- Pipelined
 - execute each instruction in multiple steps
 - perform 1 step / instruction in each clock cycle
 - process multiple instructions in parallel – assembly line




Functional Elements



- Two types of functional elements in the hardware:
 - elements that *operate on* data (called *combinational elements*)
 - elements that *contain* data (called *state* or *sequential elements*)

Combinational Elements

 - Works as an *input* \Rightarrow *output function*, e.g., ALU
- Combinational logic *reads input data from one register and writes output data to another, or same, register*
 - *read/write happens in a single cycle* – combinational element *cannot store data* from one cycle to a future one



Combinational logic hardware units

  




State Elements

- State elements contain *data* in internal storage, e.g., *registers* and *memory*
- All state elements together *define* the *state of the machine*
 - *What does this mean? Think of shutting down and starting up again...*
- *Flipflops* and *latches* are 1-bit state elements, equivalently, they are *1-bit memories*
- The *output(s)* of a flipflop or latch *always* depends on the bit value stored, i.e., its state, and can be called *1/0* or *high/low* or *true/false*
- The *input* to a flipflop or latch can change its state depending on whether it is clocked or not...




 Synchronous Logic: Clocked Latches and Flipflops




State Elements on the Datapath: Register File

■ Port implementation:

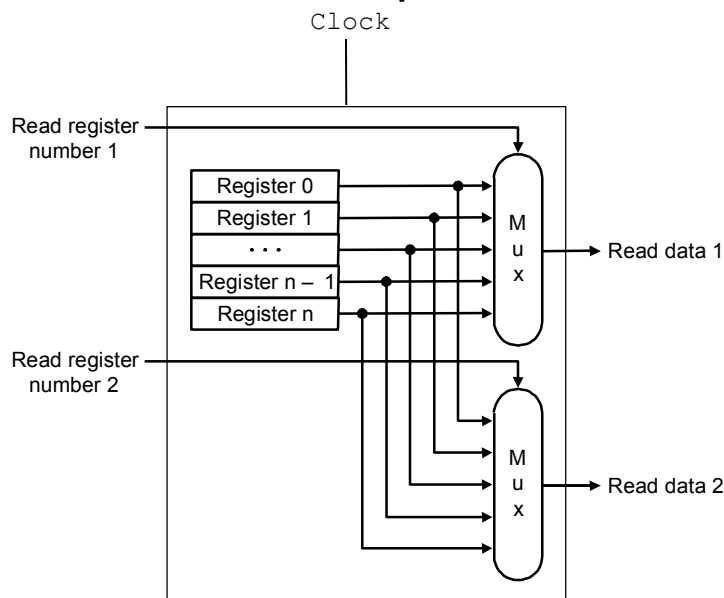


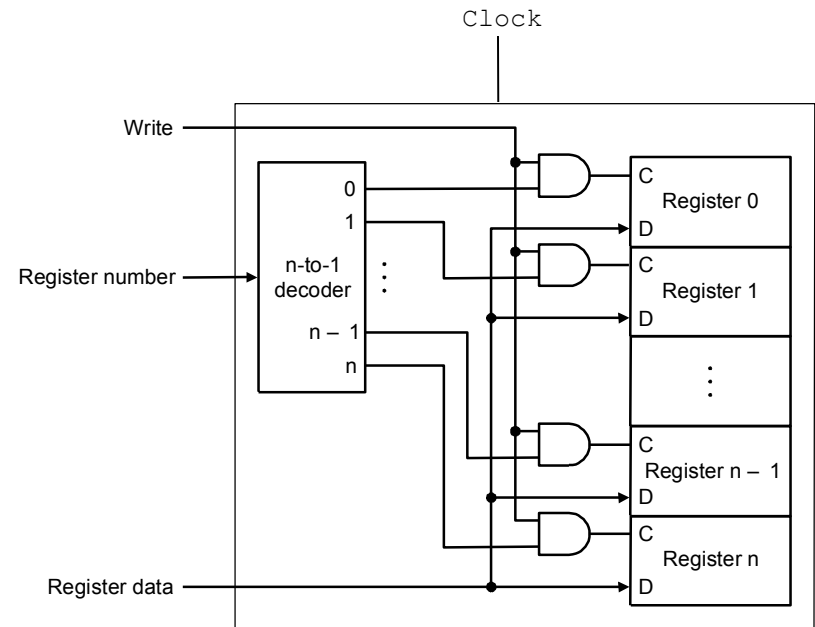Read ports are implemented with a pair of multiplexers - 5 bit multiplexers for 32 registers



Write port is implemented using a decoder - 5-to-32 decoder for 32 registers. Clock is relevant to write as register state may change only at clock edge

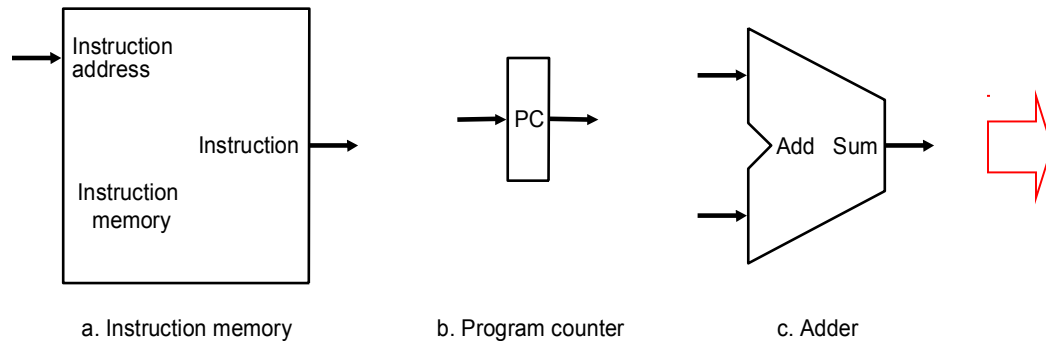Datapath: Instruction Store/Fetch & PC Increment




a. Instruction memory

b. Program counter

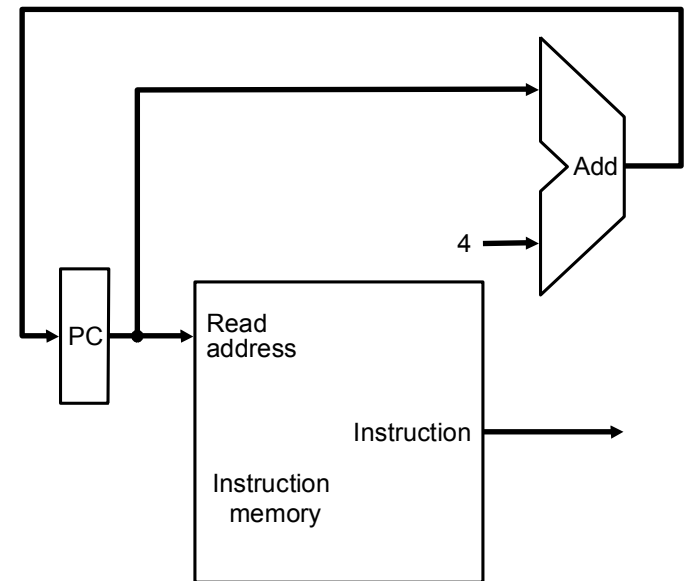
c. Adder

Three elements used to store and fetch instructions and increment the PC




Datapath


Animating the Datapath

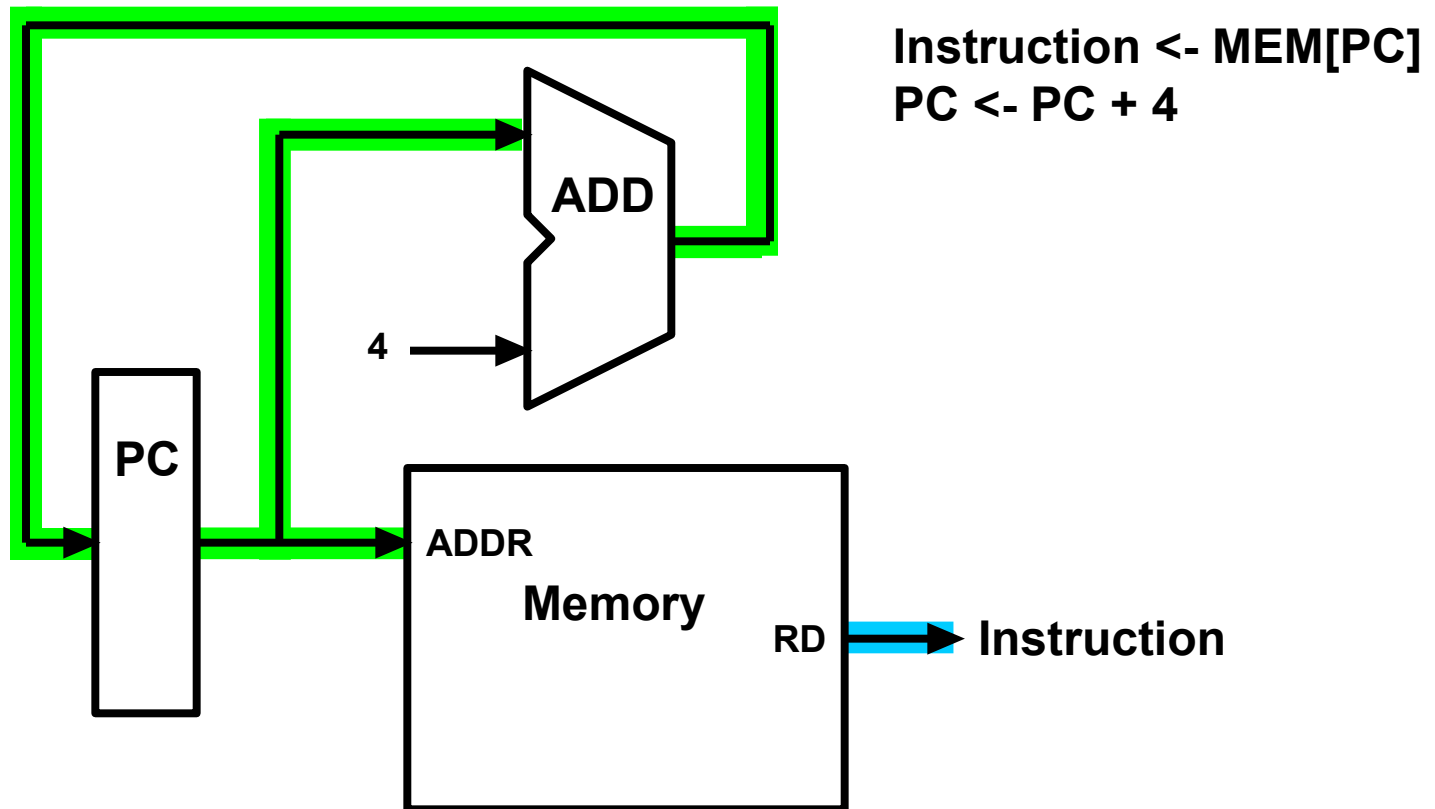


Datapath: R-Type Instruction

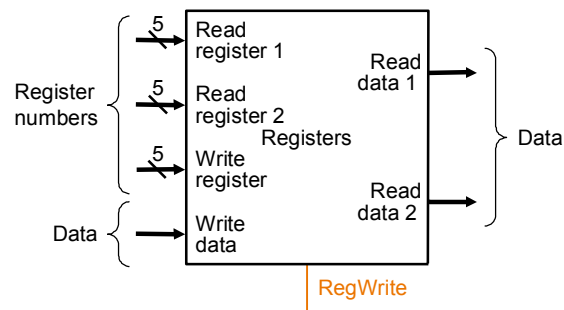

a. Registers

 

b. ALU

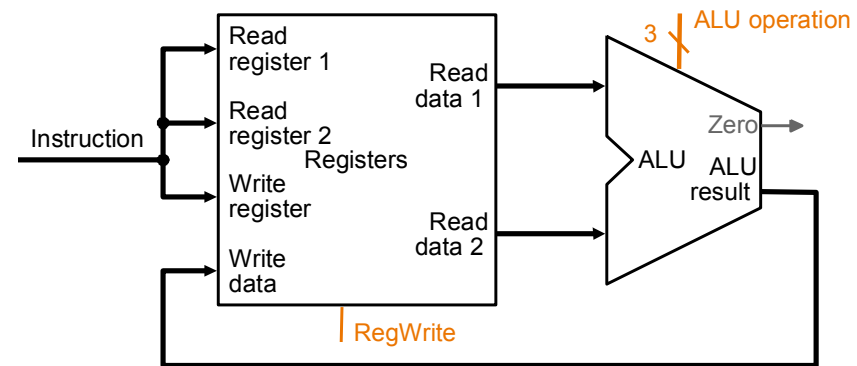

Datapath

Two elements used to implement R-type instructions


Animating the Datapath

Instruction




add rd, rs, rt

$R[rd] \leftarrow R[rs] + R[rt];$

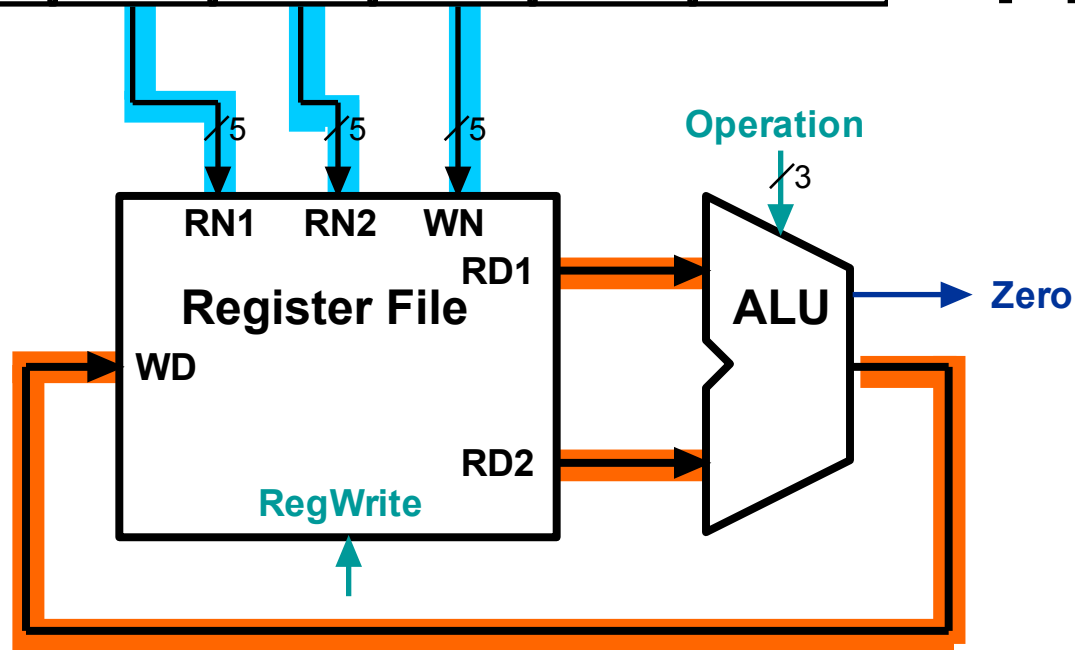


Datapath: Load/Store Instruction

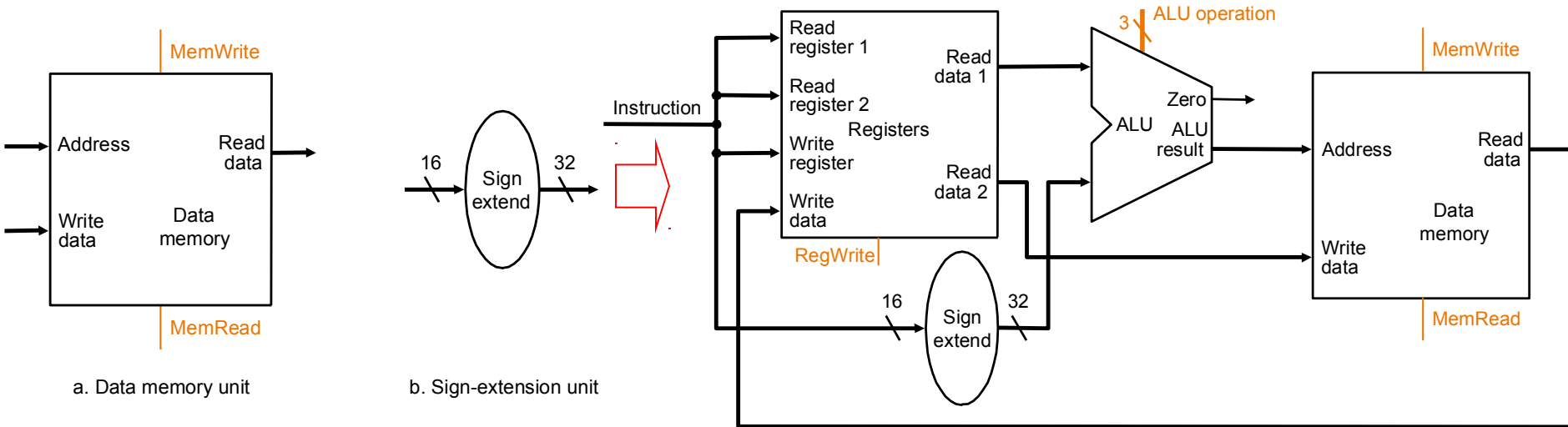

**Two additional elements used
To implement load/stores**

Datapath

Animating the Datapath

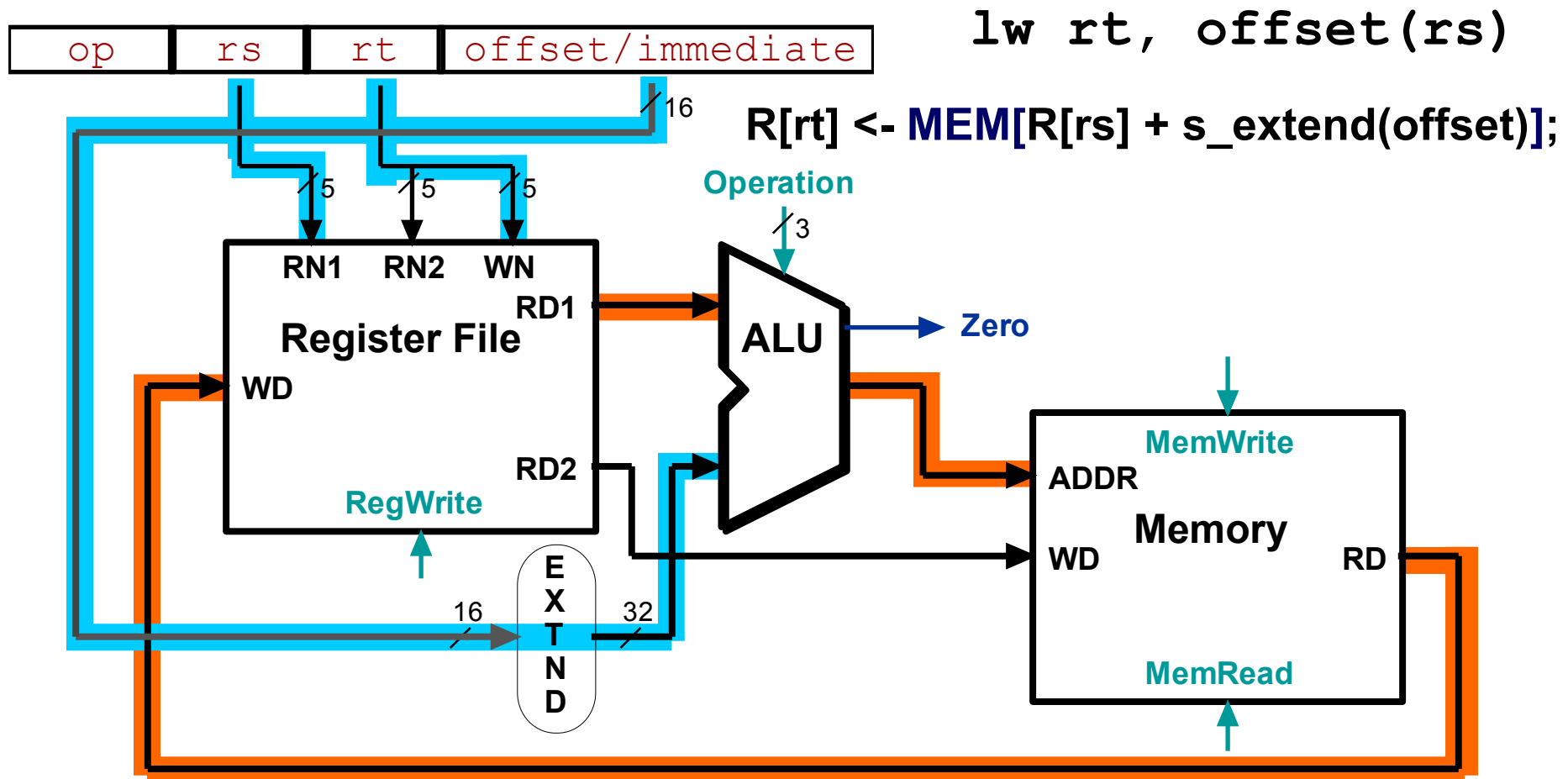

Animating the Datapath



sw rt, offset(rs)

$\text{MEM}[\text{R}[\text{rs}] + \text{sign_extend}(\text{offset})] \leftarrow \text{R}[\text{rt}]$

Operation

ALU

Zero




Register File

RegWrite

MemWrite


Memory

MemRead

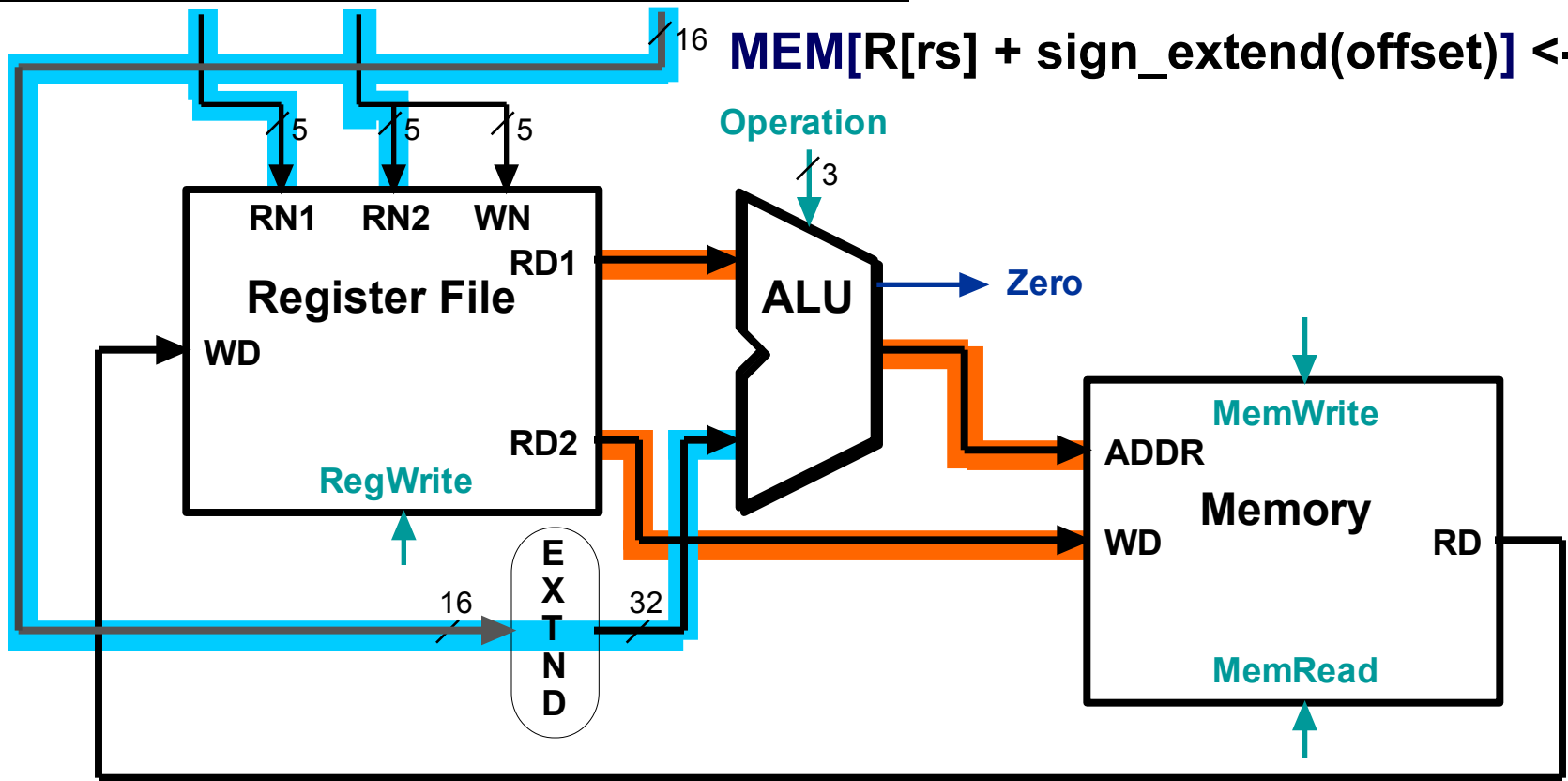  


Datapath: Branch Instruction

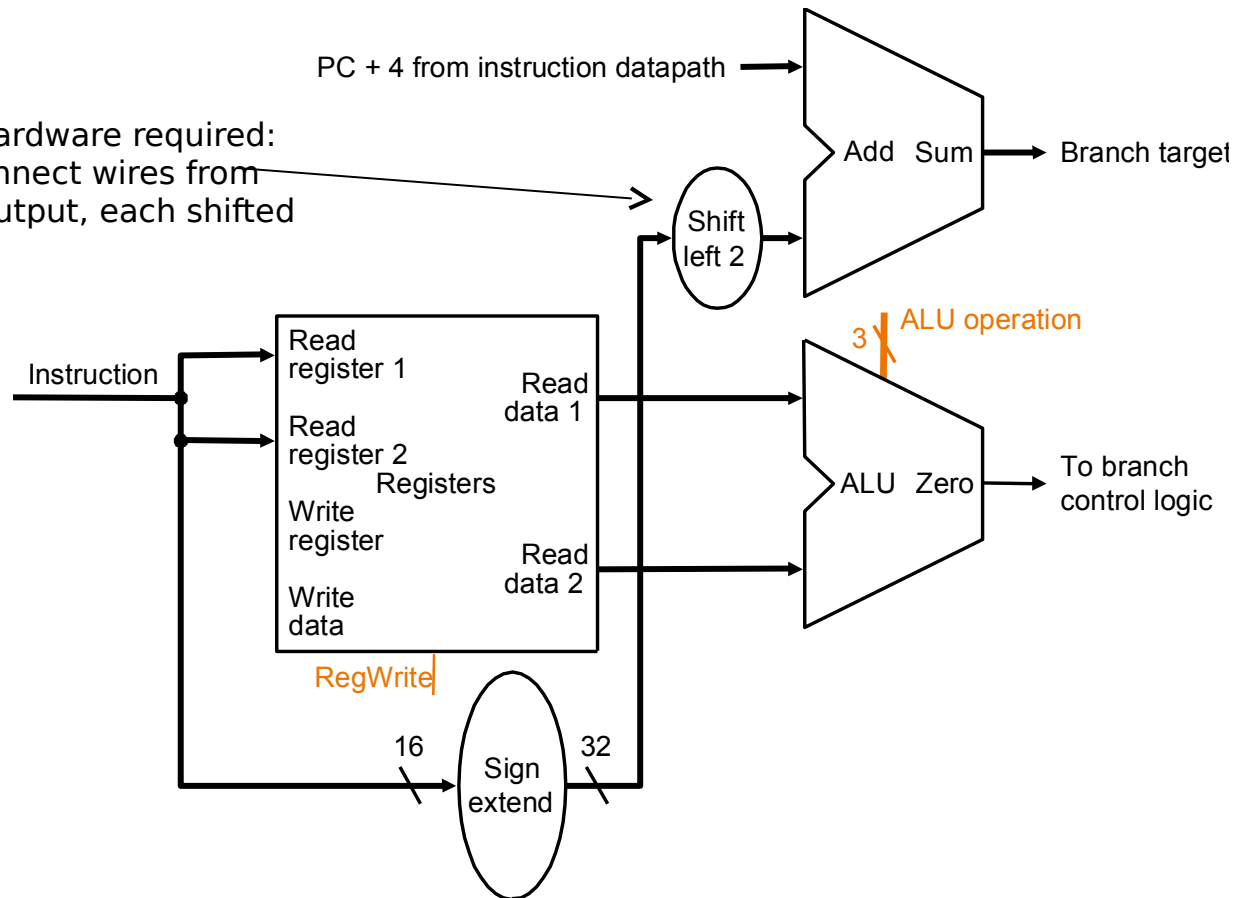No shift hardware required:
simply connect wires from
input to output, each shifted
left 2 bits




Datapath

Animating the Datapath

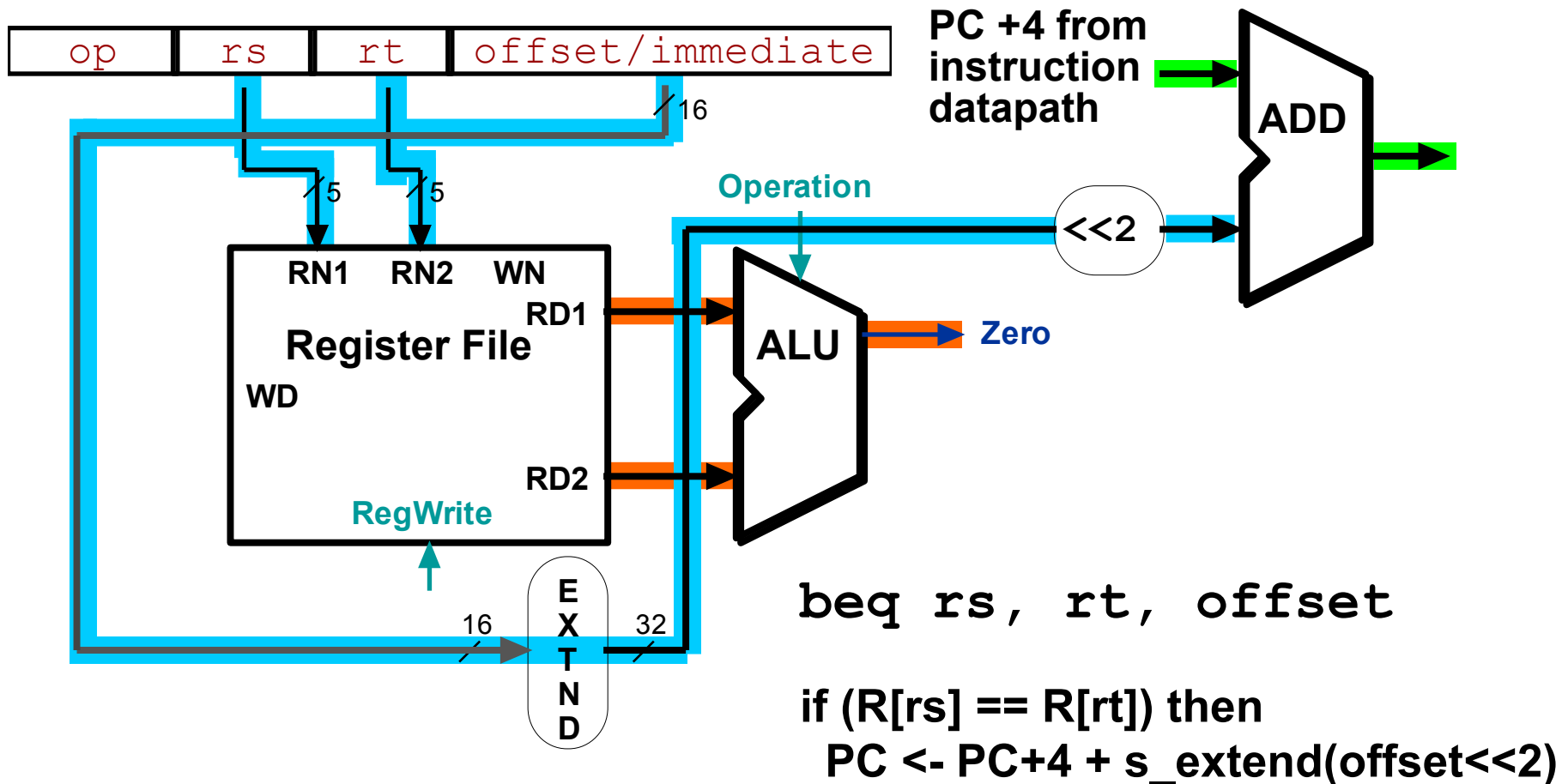

MIPS Datapath I: Single-Cycle

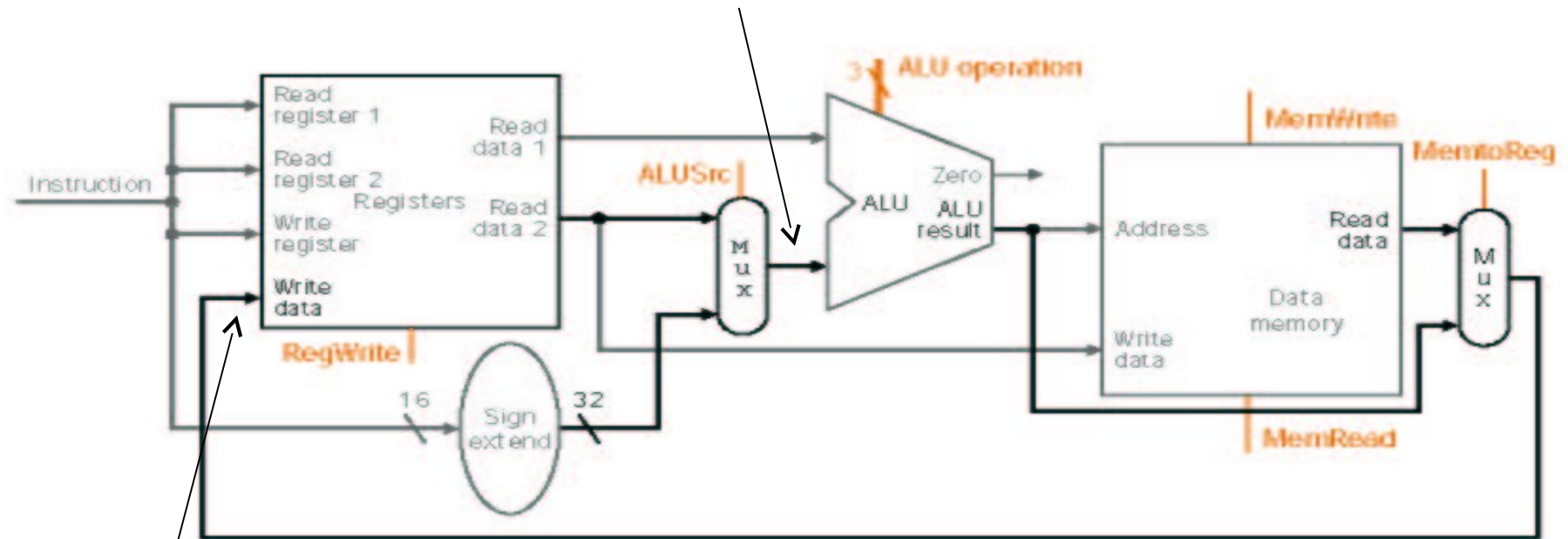
Input is either register (R-type) or sign-extended lower half of instruction (load/store)



Data is either from ALU (R-type) or memory (load)


Combining the datapaths for R-type instructions and load/stores using two multiplexors

add rd,rs,rt

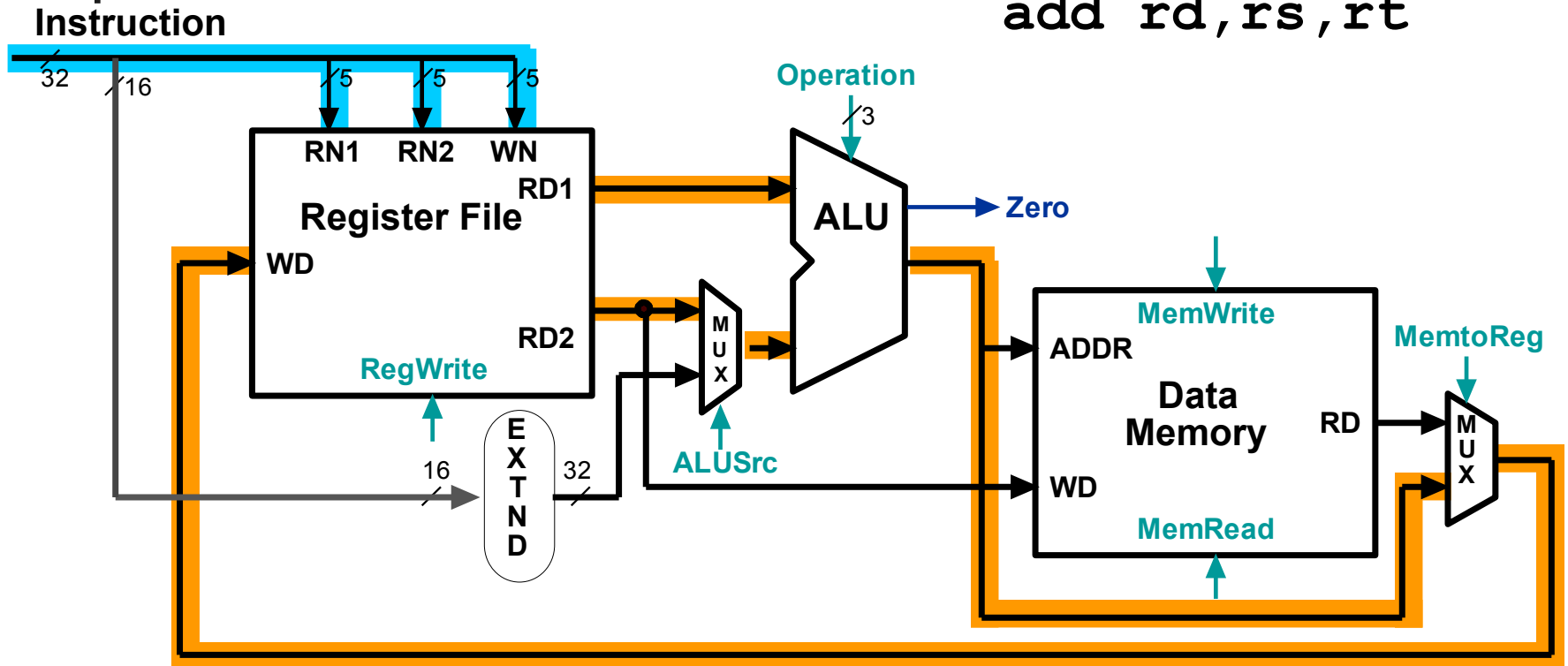


Animating the Datapath: Load Instruction

`lw rt, offset(rs)`

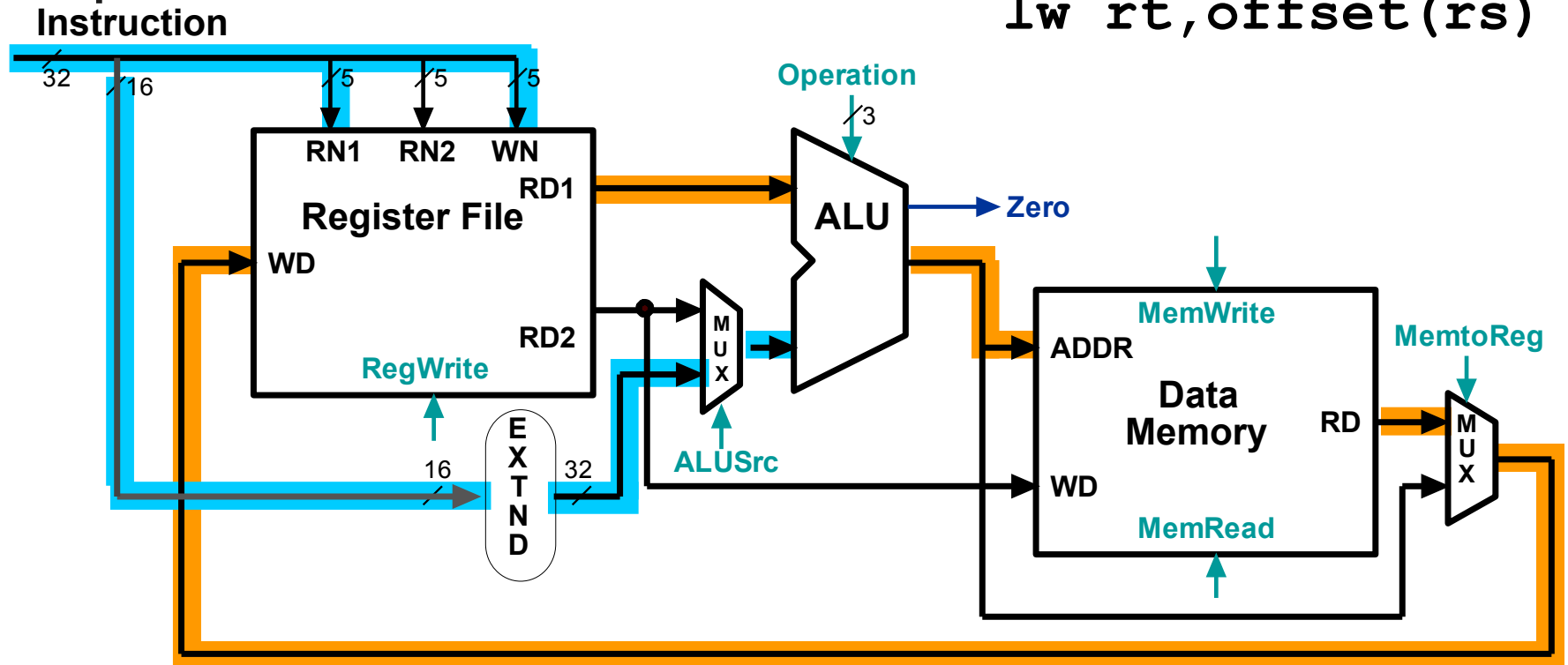


Animating the Datapath: Store Instruction


`sw rt, offset(rs)`

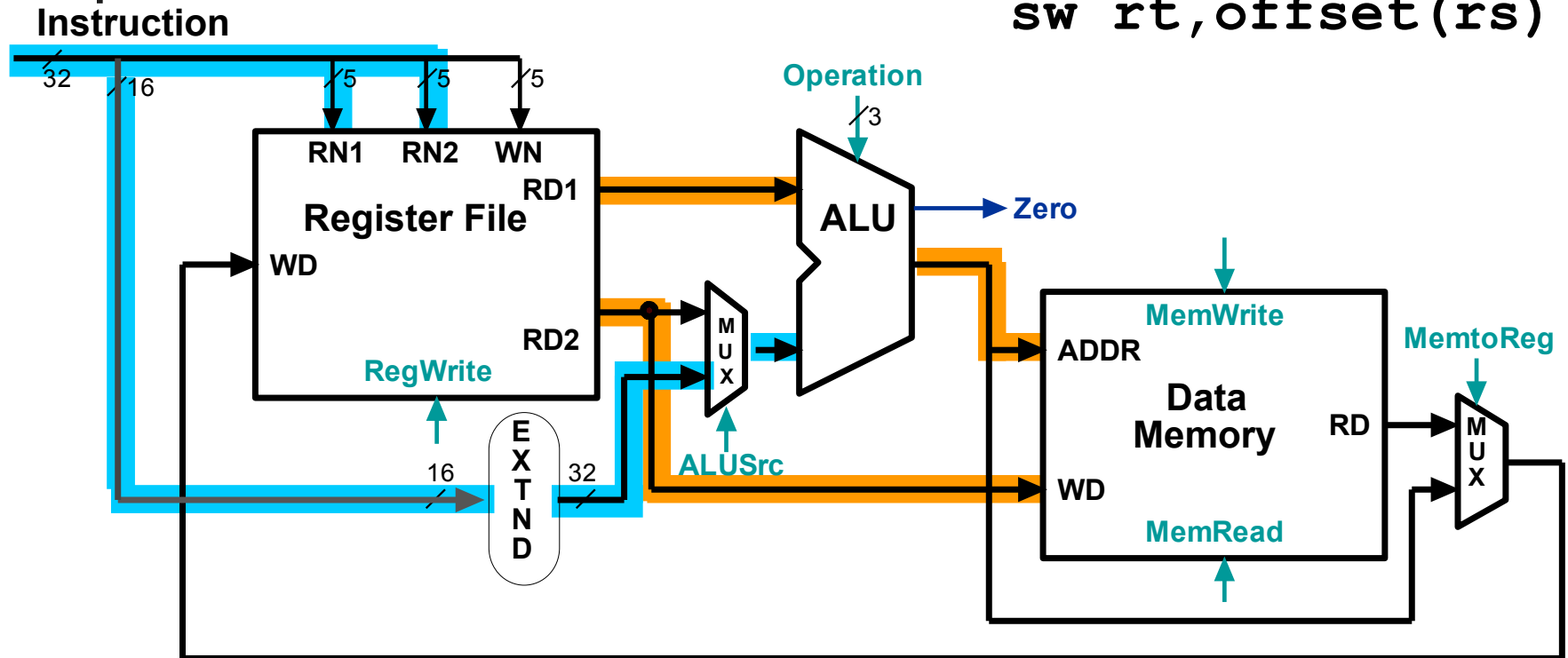

MIPS Datapath II: Single-Cycle

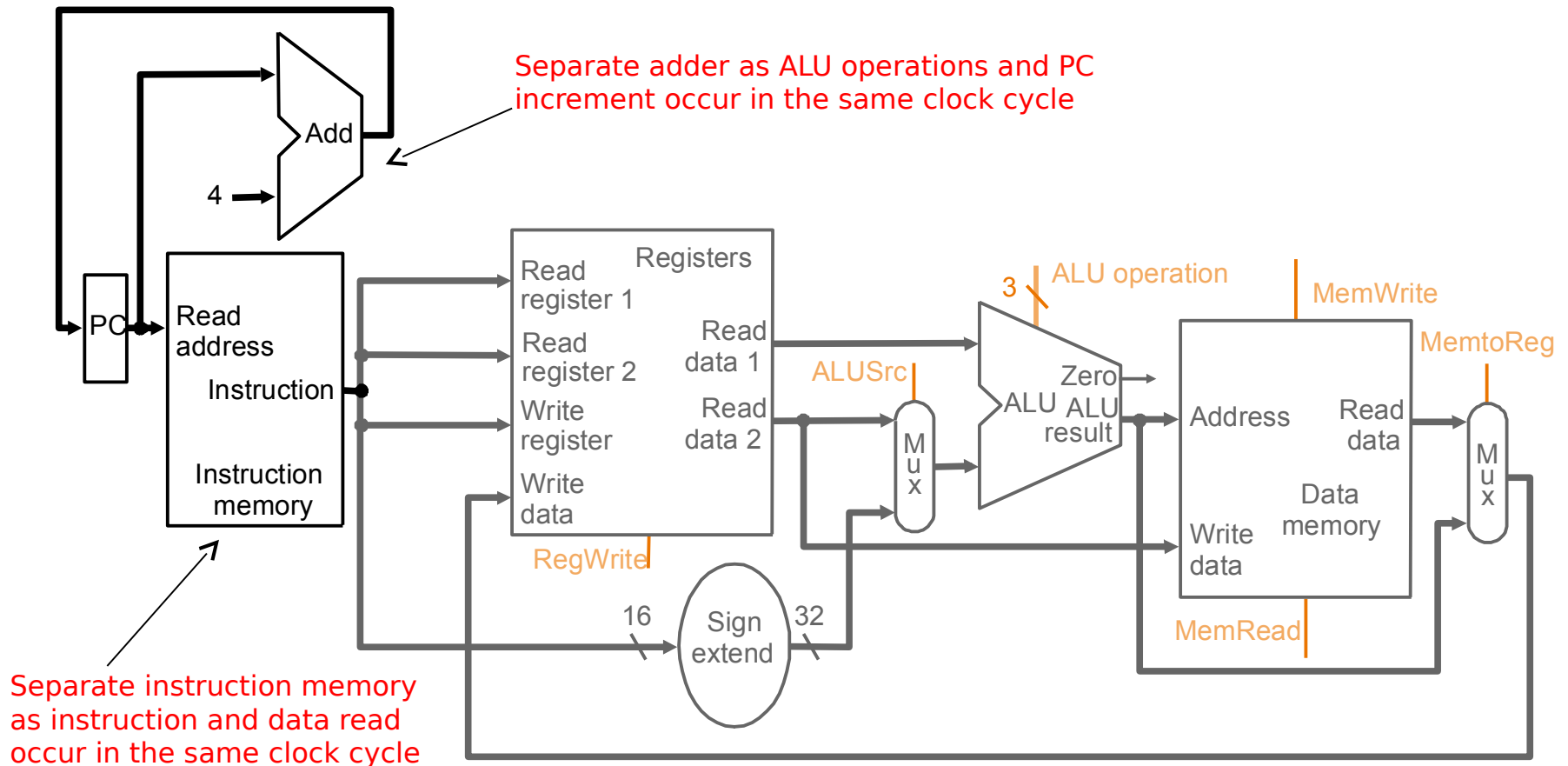


Adding instruction fetch

 


Important note: in a single-cycle implementation data cannot be stored during an instruction - it only moves through combinational logic

Datapath Executing add


`add rd, rs, rt`

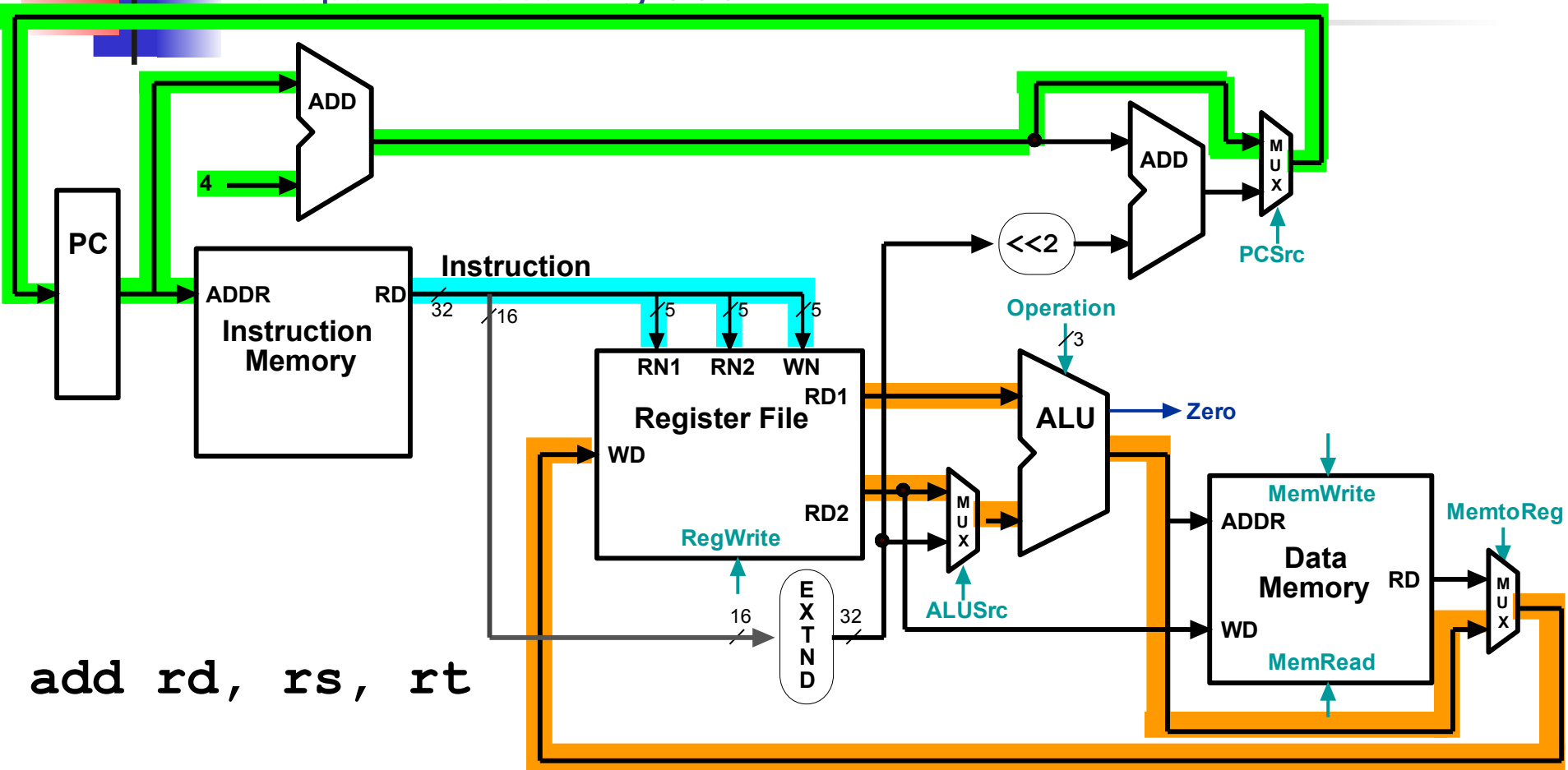

Datapath Executing lw

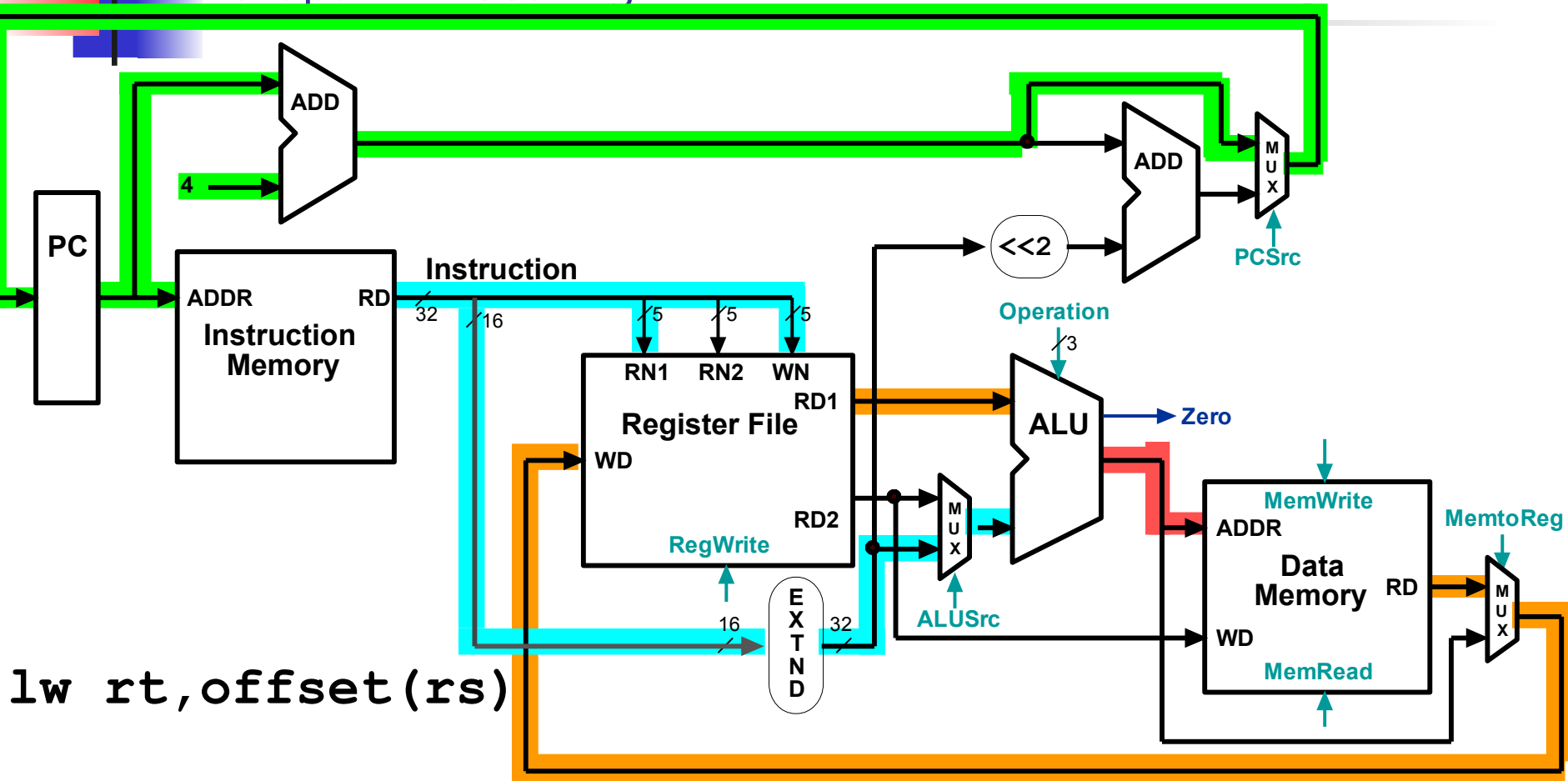

Datapath Executing sw

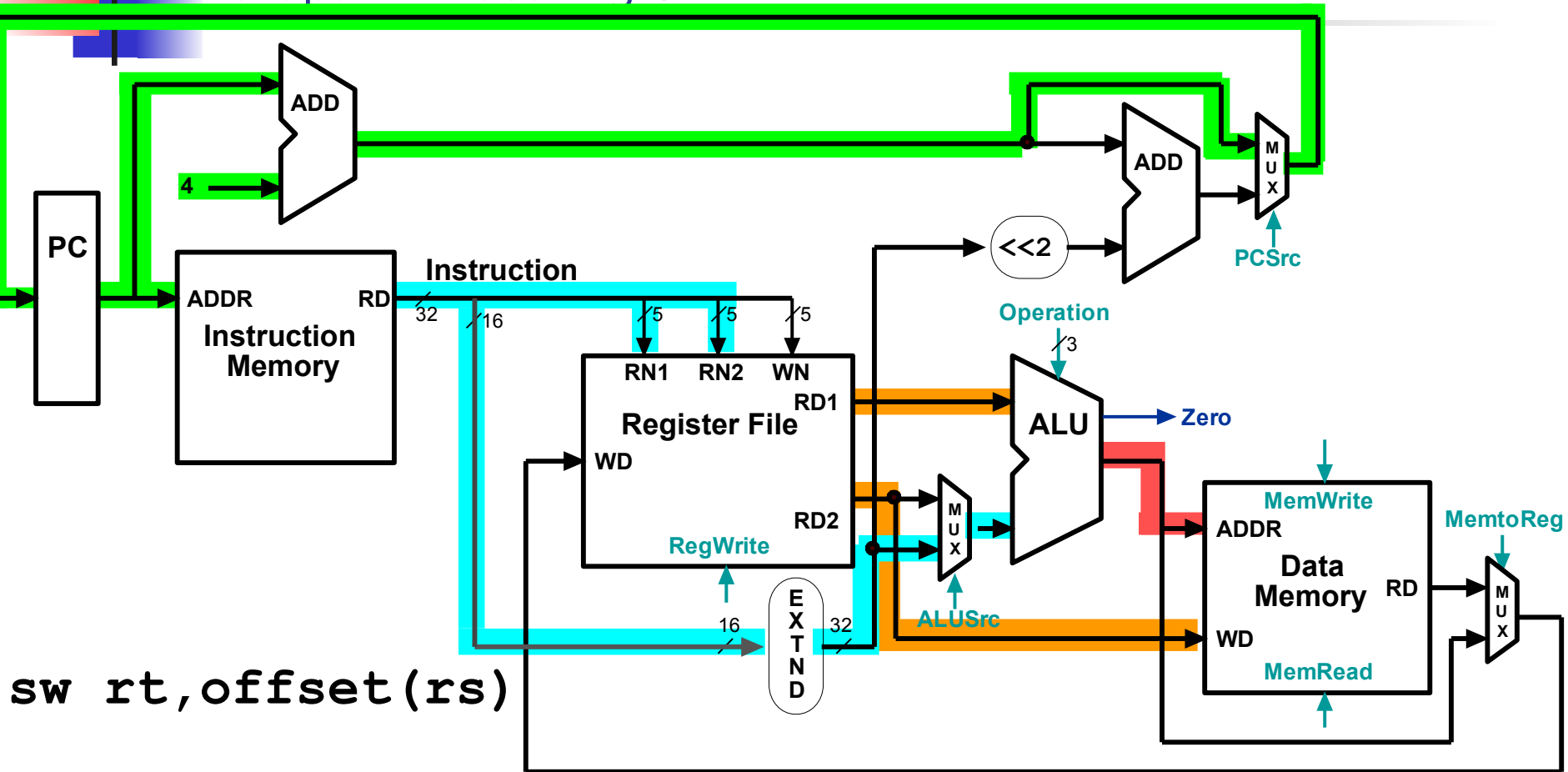

Datapath Executing beq

